

Babasaheb Ambedkar Govt Polytechnic
FEEE 1st Internal 2nd Semester
AY-2024-25 (FM-20)

1. Answer the 3 MCQs with justification(3*2=6)

- A. Input Resistance of Ideal Op-amp is **a.** 0 **b.** infinity **c.** moderately low **d.** moderately high
B. Which of the following Gate is a Universal Gate? **a.** NAND **b.** EX-OR **c.** AND **d.** NOT
C. An inductor acts as _____ circuit when DC source is applied. **a.** short **b.** open **c.** resistive
d. capacitive.

2. Answer the Following Questions(7*2=14)

A. Write Characteristics of an ideal Op-Amp.

Or

Deduce Expressions for Closed loop gain of an ideal op-amp when input is given at non-inverting terminal.

B. Draw Symbol, expression, and truth table of NAND and EXOR Gate.

Babasaheb Ambedkar Govt Polytechnic
FEEE 1st Internal 2nd Semester
AY-2024-25 (FM-20)

1. Answer the 3 MCQs with justification(3*2=6)

- A. Input Resistance of Ideal Op-amp is **a.** 0 **b.** infinity **c.** moderately low **d.** moderately high
B. Which of the following Gate is a Universal Gate? **a.** NAND **b.** EX-OR **c.** AND **d.** NOT
C. An inductor acts as _____ circuit when DC source is applied. **a.** short **b.** open **c.** resistive
d. capacitive.

2. Answer the Following Questions(7*2=14)

A. Write Characteristics of an ideal Op-Amp.

Or

Deduce Expressions for Closed loop gain of an ideal op-amp when input is given at non-inverting terminal.

B. Draw Symbol, expression, and truth table of NAND and EXOR Gate.